

An "ultra-graphics" adaptor for the VZ200/300 computers

Matthew Sorell

Are you sick of the graphics and text restrictions on your VZ200/300? Then this project is for you. Offering 256 new characters, including upper and lower case, Greek, DATA70, mathematical and other symbols, as well as graphics up to six times the normal resolution, the Ultra-Graphics extension board is a must for the serious VZ200/300 owner.

INSIDE THE VZ computer lies a very versatile video IC. Unfortunately, the designers were working on a low budget machine and so the graphics capabilities are quite limited. However, by extending the amount of video RAM used, adding a character generator EPROM and a few other ICs, the graphics capabilities of both the VZ200 and VZ300 can be fully realised.

The first problem, then, is to fit 6K of RAM into a 2K memory position. To do this, a latch was used to provide an extra two address bits to bank switch an 8K RAM into the normal 2K of video RAM space, in position 7000-77FFH (28672-30719). As an 8K RAM is used, but the highest resolution available only uses 6K, an extra 2K of general data storage RAM is available. This can be used, for example, to store character definitions for use in high resolution graphics.

The latch used was installed into I/O address 20-2FH (32-47), which is the same position as the joystick controller. However, as the joystick is a Read-Only device, a Write-Only Latch will not interfere with it. The latch also controls the new graphics and text modes.

A word of warning: This project is an extensive internal modification to the VZ200 or VZ300 computers. If you are not

confident about modifying the computer, then I recommend you do NOT attempt this project without experienced help. I also strongly recommend you obtain a copy of the "VZ300 Technical Manual", which will assist you if problems arise. Building this project also voids the manufacturer's warranty, so it's best tackled after your machine's warranty has expired.


New characters, extended graphics

The new character set is shown in Chart 1 here. It was originally designed to be compatible with the VZ word processor (tape version). Thus there is the 96 standard ASCII characters, which are slightly out of order to be more compatible with the standard VZ text. There is also a DATA70 ("computer" type) character set, a Greek character set, some international characters, and mathematical symbols which can be accessed by poking their code into video memory, or printing the correct semigraphics character in the right colour. A dedicated screen controller routine could also be used.

The new graphics modes serve many useful purposes. The highest resolution graphics mode (256 x 192 pixels), is equivalent to the resolution in text mode, and so can be used either for text, using a suitable driver routine, or for graphics,

CHART 1. The new character set. Note the addition of special symbols, Greek and maths symbols and Data 70 characters.


[illegible]

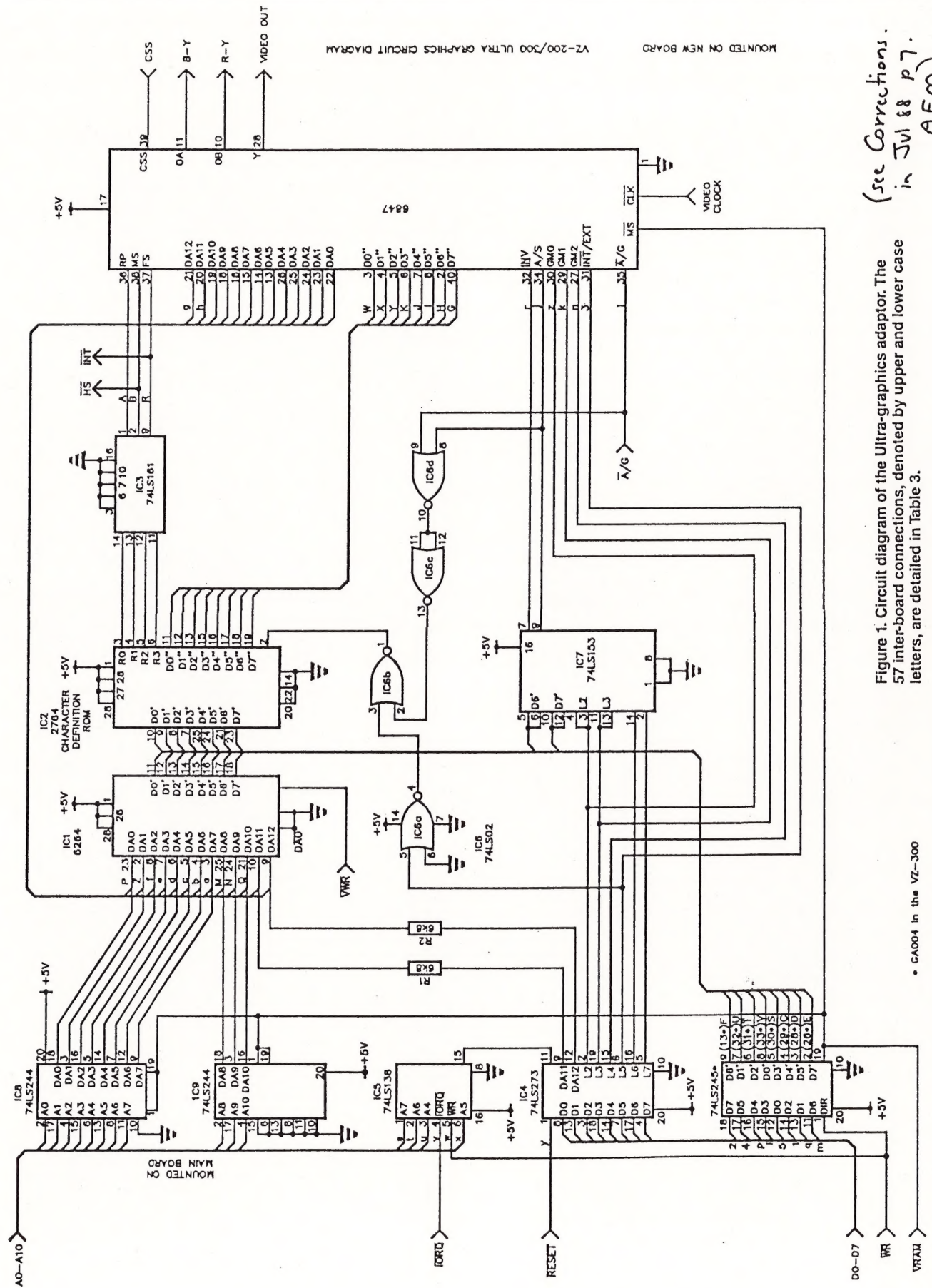

(see Corrections.
in Jul 88 p7.
AEM)


Figure 1. Circuit diagram of the Ultra-graphics adaptor. The 57 inter-board connections, denoted by upper and lower case letters, are detailed in Table 3.

• GA004 in the VZ-300

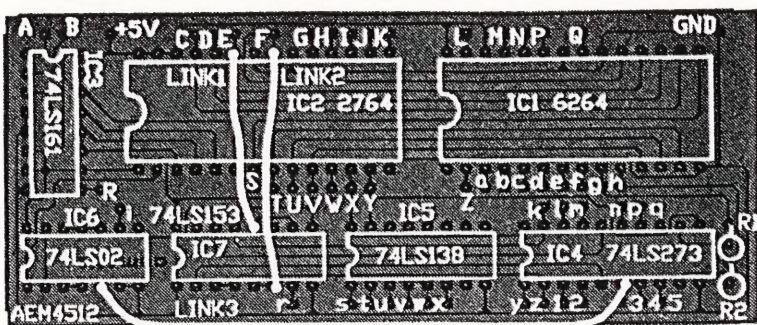

Overlay for the printed circuit board showing the placement of components and where the inter-linking wires connect. Note the links on the board.

(see Corrections. in Jul 88 p 7. AEM)

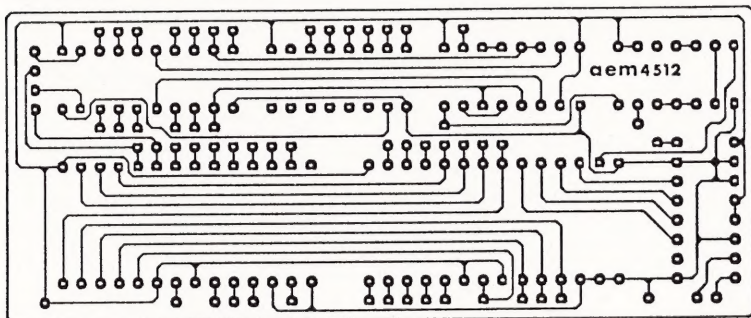

Full-size printed circuit artwork.

(see Correction in Jun 88 p 7. AEM)

such as graphs or high resolution pictures. With an analogue to digital converter, the VZ computer could be easily used as a low cost laboratory computer, able to graph results with acceptable resolution. The highest resolution colour mode (128 x 192 pixels) is also similarly useful.

It is also possible to access the 3 x 2 semigraphics in text mode, which occurs when graphics characters are called while the external character generator is enabled. For more information on the graphics and text capabilities, see the two-part feature "Screen Handling on the VZ200/300", by Bob Kitch, in the September and October 1986 issues of AEM.

CIRCUIT OPERATION

IC5 (74LS138) decodes A4-A7, IORQ and WR to recognise I/O port 20-2FH (32-47). When this occurs, pin 15 goes low, causing IC4 (74LS273) to latch the contents of the data-bus (D0-d7). This latch is cleared on RESET to ensure that text is sent to the correct memory page. DA11 and DA12 are bits 00 and 1. They provide bank switching to fit the 8K RAM into the 2K video memory allocation (7000-77FFH (28672 to 30719)). L2, L3 and L4 signals control the graphics mode pins on the 6847 video IC, L5 controls the internal/external character sets and with this the 2 x 2 (normal) or 3 x 2 semigraphics modes. L6 and L7 control whether the inverse and semigraphics modes follow bits 6 and 7 of the character code (normal) or L2 and L3 respectively.

The output of IC1 (6264) controls address lines 4 to 11 of the character EPROM. The EPROM is programmed to mirror the output of IC1 UNLESS the external character set is specifically required. In this case, pin 2 of IC2 is sent high by IC6 (74LS02), which decodes when L5 is high and the video IC is in text mode. IC7 (74LS153) multiplexes the inverse and semigraphics control lines, and is controlled by L6 and L7 to decode L2, L3, D6' and D7'.

IC3 (74LS161) is a synchronous binary counter. It counts through the external character set in the EPROM, so that the correct character row data is released.

PARTS LIST

Resistors 1/4W, 5%
R1, R2 6k8

Semiconductors

IC1 6264 8Kx8 static RAM
IC2 2764 8Kx8 Char. Set EPROM

IC3 74LS161

IC4 74LS273

IC5 74LS138

IC6 74LS02

IC7 74LS153

IC8

IC9 74LS244

Miscellaneous

AEM4512 pc board; 2 x 28-pin low profile IC sockets; thin insulated hook-up wire (ribbon cable).

Price Estimate: \$40-\$50

* A fully programmable EPROM with the character set in Chart 1 is available from:

Matthew Sorell, 41 Mills St, Clarence Pk, 5034 S.A.

for \$18 including postage.

Customised character sets are negotiable. Kit suppliers may include pre-programmed EPROMs; check with your supplier first.

Construction

The first thing to do, no matter whether you've purchased a kit or assembled your own parts and made your own printed circuit board, is to check the pc board. See that all the holes are drilled and that there are no broken tracks or tiny copper 'bridges' between the closely-spaced IC pads. Correct any problems you find.

You can commence assembly by first installing the resistors, IC sockets and the non-socketed ICs into the printed circuit board, as shown in the overlay diagram here. The three links should be made on the solder side of the board using insulated wire. Now install the 57 interconnecting wires as required. Make these about 150-200 mm long for the time being. The wire used should be as thin as possible. Separated ribbon cable is quite suitable. The wires should be connected through the component side of the pc board.

Now open the computer by removing the six screws underneath. Remove the main board by undoing the four screws holding it in. Be careful not to flex the keyboard cable too much; if it breaks, it's the devil's own job fixing it. Note which wires go to the power switch and the loudspeaker, then desolder these, leaving the wires on the main pc board.

Desolder the RF shield covering the main board. Use solder wick to do this. Remove the 6116 RAM on the main board, near the TV modulator. The best way to do this is to cut the pins on one side of the IC and wobble it on the other side until the rest of the pins break. Just make sure you've got the right chip! Now remove the pin stubs left in the pc board. ▶

LEVEL

We expect that constructors of an

INTERMEDIATE

level, between beginners and experienced persons, should be able to successfully complete this project.

TABLE 1. VZ200 — tracks to cut.

IC	Pin # to	IC	Pin# Position
6847	29	+5V	- Adjacent to pin 29 (top side)
6847	32	6847	2 Under 6847 (solder side)
6847	34	6847	40
6847	40	74LS245	2 Between ICs (solder side)
6847	8	74LS245	3 Between ICs (solder side)
6847	7	74LS245	4 Between ICs (solder side)
6847	6	74LS245	5 Between ICs (solder side)
6847	5	74LS245	6 Between ICs (solder side)
6847	4	74LS245	7 Between ICs (solder side)
6847	3	74LS245	8 Between ICs (solder side)
6847	2	74LS245	9 Between ICs (solder side)
6847	27	Ground	Lift pin out of PCB
6847	38	Ground	Lift pin out of PCB
6847	31	Ground	Lift pin out of PCB

TABLE 2. VZ300 — tracks to cut.

IC	Pin# to	IC	Pin# Position
6847	32	GA004	27 Under 6847 (solder side)
6847	3	GA004	33 Under 6847 (solder side)
6847	4	GA004	32 Under 6847 (solder side)
6847	5	GA004	31 Under 6847 (solder side)
6847	6	GA004	30 Under 6847 (solder side)
6847	7	GA004	29 Under 6847 (solder side)
6847	8	GA004	28 Under 6847 (solder side)
6847	34	GA004	26 Under 6847 (solder side)
6847	40	6847	34 Under 6847 (solder side)
6847	2	6847	32 Under 6847 (solder side)
6847	27,30,31	Ground	- Cut, separate and remove track under 6847 (solder side)
6847	29	+5V	Lift pin out of PCB

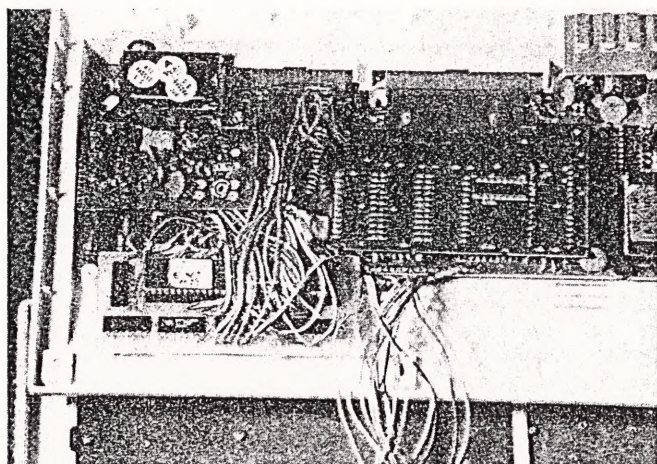


Photo 1. The Ultra-Graphics board installed in the VZ200.

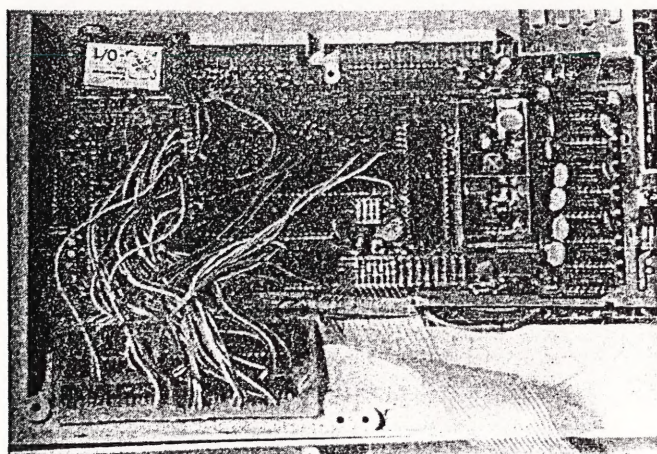


Photo 2. The Ultra-Graphics board installed in the VZ300.

TABLE 3. Interboard connections.

Wire #	VZ-200 IC	Pin #	VZ-300 IC	Pin #
A	6847	36	6847	36
B	6847	38	6847	38
+5V	SUPPLY RAIL		SUPPLY RAIL	
C	74LS245	4	GA004	29
D	74LS245	3	GA004	28
E	74LS245	2	GA004	26
F	74LS245	9	GA004	27
G	6847	40	6847	40
H	6847	2	6847	2
I	6847	8	6847	8
J	6847	7	6847	7
K	6847	6	6847	6
L	(6116)	21	(6116)	21
M	(6116)	23	(6116)	23
N	(6116)	22	(6116)	22
P	(6116)	8	(6116)	8
Q	(6116)	19	(6116)	19
GND	74LS245	10	SUPPLY RAIL	
R	6847	37	6847	37

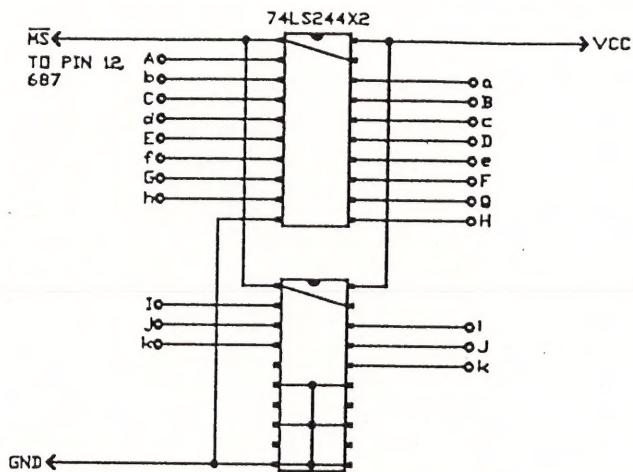


Figure 3. Wiring of the 74LS244 buffers – wrap them in insulation tape once you've got your computer working again.

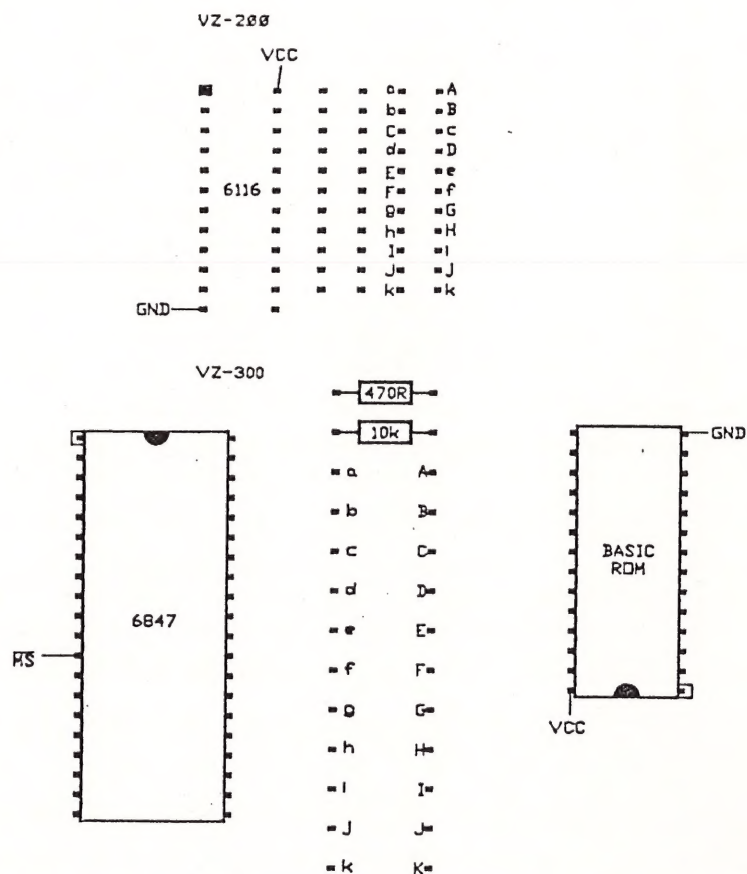


Figure 4. Showing the connection points for the 74LS244 buffers into the VZ200 and 300.

S	74LS245	5	GA004	30	l	74LS245	15	GA004	10
T	74LS245	6	GA004	31	m	74LS245	11	GA004	13
U	74LS245	7	GA004	32	n	6847	27	6847	27
V	74LS245	8	GA004	33	p	74LS245	16	GA004	11
W	6847	3	6847	3	q	74LS245	13	GA004	8
X	6847	4	6847	4	r	6847	32	6847	32
Y	6847	5	6847	5	s	I/O Connector	29	Z80(780C)	37
Z	(6116)	7	(6116)	7	t	I/O Connector	12	Z80(780C)	36
a	(6116)	1	(6116)	1	u	I/O Connector	27	Z80(780C)	34
b	(6116)	2	(6116)	2	v	I/O Connector	5	Z80(780C)	20
c	(6116)	3	(6116)	3	w	I/O Connector	14	Z80(780C)	22
d	(6116)	4	(6116)	4	x	I/O Connector	10	Z80(780C)	35
e	(6116)	5	(6116)	5	y	74LS04	4	Z80(780C)	26
f	(6116)	6	(6116)	6	z	6847	30	6847	30
g	6847	21	6847	21	1	74LS245	14	GA004	9
h	6847	20	6847	20	2	74LS245	18	GA004	14
i	6847	35	6847	35	3	6847	31	6847	31
j	6847	34	6847	34	4	74LS245	17	GA004	12
k	6847	29	6847	29	5	74LS245	12	GA004	7

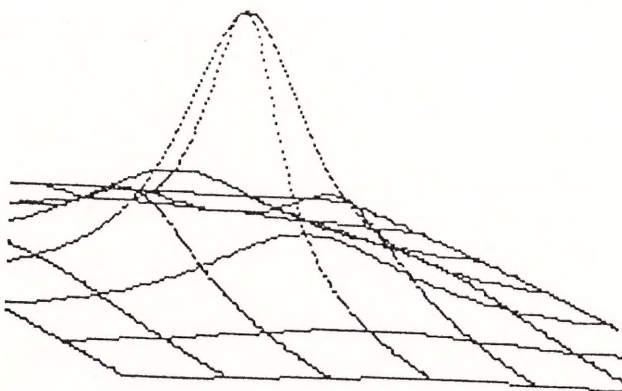


Figure 2. Three-dimensional graphics!

This method greatly reduces overheating problems. Missing tracks are an absolute no-no in computers!

In the VZ200, undo the two screws holding the PAL converter module behind the TV modulator and lift up, to reveal the 6847 video IC. There are two plastic screw mounts on the base of the VZ200. These should be broken off with pliers.

Now the fun begins! Cut the tracks listed in Table 1 (VZ200) or Table 2 (VZ300). Identify each track carefully! Note several IC pins are lifted. When doing this, heat them with a soldering iron and lever the pin out using a small precision screwdriver. Be careful not to break the pin at the IC or all will be lost! Clip off the narrow part of the pin.

Position the Ultra-graphics board in its approximate location relative to the main board. See Photo 1 (VZ200) or Photo 2 (VZ300). Connect each wire in order, as in Table 3, to the main printed circuit board on the component side. Cut the wires with a little leeway (about 10 mm longer than required). Tick each connection in Table 3 as it is made, to avoid errors.

Check and recheck all connections. Reconnect the loudspeaker and power switch, fit the main board back into the box (no screws yet) and the new board alongside, as in the photos. Plug in the RAM and EPROM, the video and power supply cables, and switch on. The display should be almost normal. Some characters may be incorrect. The computer should otherwise work correctly. If not, then check for short and open circuits, incorrectly oriented components, and incorrect inter-board wiring.

Unfortunately, the Z80 has trouble controlling the address lines through the resistor buffer with this new board, making the graphics only about 90% accurate. To correct this, power down and then remove the eleven 6k8 resistors on the main board (in the VZ300, do not remove the adjacent 10k and 470R resistors). Wire up IC8 and IC9 (74LS244) as shown in

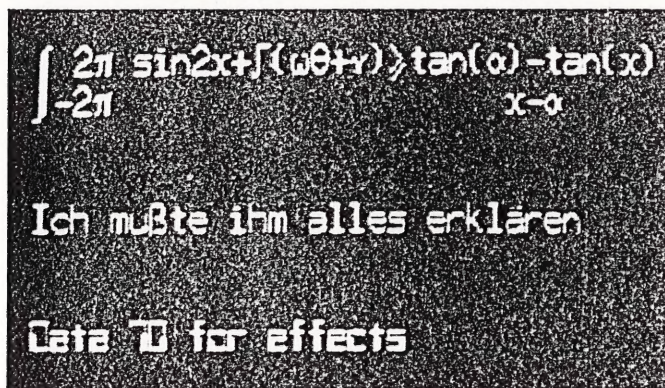


Photo 5. A small taste of what is now possible with text: mathematics, German and Data 70 characters.

Figure 3. Clip the narrow part of each pin, and connect these ICs to the board via short (20 mm) pieces of wire, longer for the power supply and enable signal. Connect them as shown in Figure 4. Wrap these ICs in insulation tape. Switch the computer back on, and when the computer is working, check the new board by typing in:

```
10 CLS:POKE 30744,96:OUT 32,224
20 FOR A=0 TO 255
30 POKE 28672+A,A
40 NEXT
50 PRINT @256,""
```

and running this little program. The new external character set should be displayed.

Screw the board into the box, and the cover on top. Voila. Ultra-Graphics!

The RF shield can be reinstalled, but creates a few problems with mounting the new board. It is not essential for the computer's operation and can be left out if you wish.

Applications

It's no use having a set of useful new features without suitable applications with which to exploit them.

The Word Processor

The character set has been designed to be used in conjunction with the tape version of the word processor. Not having used the cartridge version, I don't know how the new character set should be enabled, or if it is compatible with this word processor. To enable a suitable character set, type in:

```
POKE 30744,96:OUT 32,160
```

before loading the word processor. Upper and lower case will be enabled, and semigraphics characters will be used as markers. You will find that the word processor is now considerably easier to use.

Text in BASIC

When using the external character set with BASIC, the white-on-black screen should be enabled. BASIC revision 1.2 uses only this mode, but version 2.0 boots up in black-on-white (inverse mode). Since characters 96 to 127 are non-standard, the white-on-black mode should be enabled by typing POKE 30744,96; or by keeping CTRL depressed when turning the computer on.

As mentioned earlier, characters 128-255 can be accessed by poking the correct code onto the screen, or by printing the correct graphics character in the correct colour. This is how photo six was produced. Characters 64 to 127 can be accessed as inverse characters. The character sets available are listed in Table 5.

Using Graphics

The computer now boots in graphics mode 0, so before any commercial software (games) can be loaded, you should type in:

```
OUT 32,8
```

to enable the normal graphics mode.

If you have a GP-80 printer, which is compatible with the graphics dump screen, then it is possible to dump games screens by playing the game in graphics mode 6 (128 x 192) on the second RAM page (OUT 32,25). Connect a reset pushbutton to ground on pin 13 (VZ200) or pin 11 (VZ300) of the 74LS04. Reset the computer at a suitable point in the program, and print the screen by typing in:

```
MODE (1):OUT 32,25: COPY:OUT 32,0
```


Using Extension Graphics

The following graphics modes are available:

GM0 OUT 32,0	64x64	Colour	1024 Bytes
GM1 OUT 32,4	128x64	Monochrome	1024 Bytes
GM2 OUT 32,8	128x64	Colour	2048 Bytes
GM3 OUT 32,12	128x96	Monochrome	1536 Bytes
GM4 OUT 32,16	128x96	Colour	3072 Bytes
GM5 OUT 32,20	128x192	Monochrome	3072 Bytes
GM6 OUT 32,24	128x192	Colour	6144 Bytes
GM7 OUT 32,28	256x192	Monochrome	6144 Bytes

The COLOUR command is valid for all colour modes. To set or reset a pixel in each mode, in mode 1, refer to Table 4. To clear the screen in modes 4 to 7, MODE(1) must be enabled on all RAM pages used. This means that the GM7 screen is cleared by using:

OUT 32,30:MODE(1):OUT 32,29:MODE(1):OUT 32,28:MODE(1)

The method is similar for the other modes. A three dimensional plot, based on a Microbee program, but using Graphics Mode 7 instructions is reproduced here.

Listing 1 is a graphics dump routine for Graphics mode 7, written for Shinwa-compatible dot matrix printers, such as the BMC BX-80. The author would appreciate hearing from anyone writing applications software for this graphics modification.

TABLE 4. SET/RESET in graphics modes.

GM0:	SET(X+64*(Y AND 1),INT(Y/2))
	RESET(X+64*(Y AND 1),INT(Y/2))
GM2:	SET(X,Y)
	RESET(X,Y)
GM4:	OUT 32,16+INT(Y/64)AND1:SET(X,Y AND 63)
	OUT 32,16+INT(Y/64)AND1:RESET(X,Y AND 63)
GM6:	OUT 32,24+INT(Y/64)AND3:SET(X,Y AND 63)
	OUT 32,24+INT(Y/64)AND3:RESET(X,Y AND 63)
GM1:	A=28672+INT(X/8)+16*Y
SET:	POKE A,PEEK(A) OR 2*(7 AND (NOT X))
RESET:	POKE A,PEEK(A) AND (NOT 2*(7 AND (NOT X)))
GM3:	Same as GM1
GM5:	OUT 32,28+INT(Y/64)AND1
	Then same as GM1
GM7:	OUT 32,28+INT(Y/64)AND3:A=28672+INT(X/8)+32*(YAND63)
	Then same as GM1

```

10 REMARKABLE GM7 GRAPHICS DUMP      BY MATTHEW SORELL 17/1/88
20 REM FIND TOP OF MEMORY
30 TM=PEEK(30897)+256+PEEK(30898):TM=TM-281:TL=TM-65536
40 POKE30897,(TL AND 255):POKE30898,TM/256
50 REM PUT PROGRAM AT T.O.M.
60 TM=TM+1:IF TM>32767 THEN TL=TM-65536 ELSE TL=TM
70 FOR A=TL TO TL+280
80 READ D:POKE A,D:NEXT
90 'CORRECT ABSOLUTE ADDRESSES
100 FOR I=1 TO 280
110 READ A,D:POKE TL+A,(TL+D)AND255:POKE TL+A+1,(TM+D)/256:NEXT
120 POKE30862,TL AND255:POKE30863,TM/256
130 REM X=USR(0) STARTS DUMP
140 CLEAR 50:END
150 'MACHINE CODE DATA
160 DATA245,197,229,62,27,285,186,58,62,49,285,186,58,62,13,285
170 DATA186,58,175,58,0,0,198,28,211,32,175,58,0,0,62,13,285
180 DATA186,58,62,27,285,186,58,62,75,285,186,58,175,58,0,0
190 DATA58,62,2,285,186,58,175,58,0,62,7,58,0,0,175,58,0,0
200 DATA175,58,0,0,33,0,112,237,75,0,0,283,56,48,2,283,249,9,58
210 DATA280,192,7,7,7,7,7,9,6,0,9,58,0,0,71,62,1,7,16,253,166
220 DATA48,22,58,0,0,237,68,198,3,7,71,62,3,7,16,253,71,58,0,0
230 DATA128,58,0,0,58,0,0,68,254,4,32,185,58,0,0,285,186,58,285
240 DATA186,58,58,0,0,61,254,255,32,168,58,0,0,68,254,32,32,147
250 DATA58,0,0,68,254,16,194,0,0,58,0,0,68,254,3,194,0,0,6,8
260 DATA62,13,285,186,58,16,251,225,193,241,281,0,0,0,0,0
270 'ABSOLUTE ADDRESS CORRECTION DATA
280 DATA28,197,28,196,56,195,61,198,65,199,69,288,76,195,66,288
290 DATA98,198,118,288,125,199,129,199,132,288,148,199,149,198
300 DATA157,195,165,196,171,27,174,197,188,19


```

LISTING 1

TABLE 5. Useful OUT expressions (OUT 32,N).

N	GM	Page	Chr 0-63	Chr 64-127	Chr 128-192	Chr 192-255
8	8	8	IntNorm	IntInv	SG4	SG4
4	1	8	IntNorm	IntInv	SG4	SG4
8	2	8	IntNorm	IntInv	SG4	SG4
12	3	8	IntNorm	IntInv	SG4	SG4
16	4	8	IntNorm	IntInv	SG4	SG4
17	4	1	-	-	-	-
28	5	8	IntNorm	IntInv	SG4	SG4
21	5	1	-	-	-	-
24	6	8	IntNorm	IntInv	SG4	SG4
25	6	1	-	-	-	-
26	6	2	-	-	-	-
28	7	8	IntNorm	IntInv	SG4	SG4
29	7	1	-	-	-	-
38	7	2	-	-	-	-
32	8	8	ExtNorm	ExtInv	SG6	SG6
64	8	8	IntNorm	IntInv	IntNorm	IntInv
72	2	8	SG4	SG4	SG4	SG4
96	8	8	ExtNorm	ExtInv	ExtNorm	ExtInv
184	2	8	SG6	SG6	SG6	SG6
128	8	8	IntNorm	IntNorm	SG4	SG4
132	1	8	IntInv	IntInv	SG4	SG4
168	8	8	ExtNorm	ExtNorm	SG6	SG6
164	1	8	ExtInv	ExtInv	SG6	SG6
192	8	8	IntNorm	IntNorm	IntNorm	IntNorm
196	1	8	IntInv	IntInv	IntInv	IntInv
224	8	8	ExtNorm	ExtNorm	ExtNorm	ExtNorm
228	1	8	ExtInv	ExtInv	ExtInv	ExtInv
Int=Internal Chr Inv=Inverted Text Norm=Normal Text						
SG4=2x2 Graphics SG6=3x2 Graphics Ext=External Chr						

OOPS! The pc board artwork for the AEM4512 VZ Ultra-
Graphics Adaptor was reproduced upside-down with the
board number right-reading. Strange?
Here it is, the correct way.

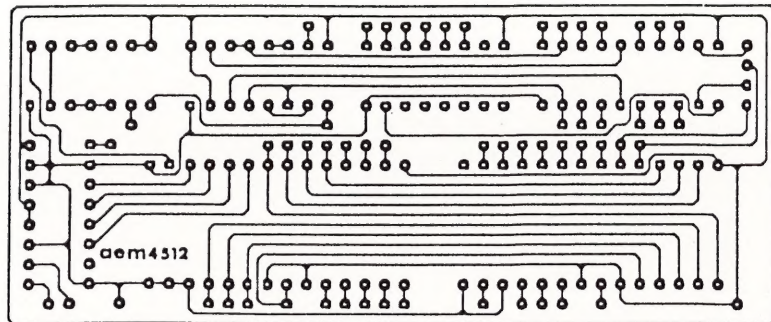

June 1988 — Australian Electronics Monthly — 7

Project 4512, VZ "Ultra-Graphics Adapter", April '88. On the
overlay, 'V' goes to pin 10 of IC2 (the 2764) and 'J' is missing — it goes
to a pad just above pin 9 of IC7 (the LS153), presently obscured by
the point of the V. On the circuit (p.58), IC3 (the LS161) has pins 3, 6,
7, 10 and 16 shown earthed when they go to +5V, while pins 4,5 and
8 were omitted — they go to earth.

July 1988 — Australian Electronics Monthly — 7

8 £ 8.